

**QUESTION # 1**

**(a)**

 


Fig. 2.17: Circuit to be implemented.

---

**Truth Table of the circuit shown in Fig. 2.17 is:**

$$X = C' \oplus (a+b)$$

$$Y = [(a+b) \oplus (a.b)'] \cdot [a+b]$$

A	B	C	$\overline{C}$	A+B	A.B	$\overline{A.B}$	$\overline{C} \oplus (A+B)$	$(A+B) \oplus \overline{A.B}$	$[(A+B) \oplus \overline{A.B}] . [A+B]$
0	0	0	1	0	0	1	1	1	0
0	0	1	0	0	0	1	0	1	0
0	1	0	1	1	0	1	0	0	0
0	1	1	0	1	0	1	1	0	0
1	0	0	1	1	0	1	0	0	0
1	0	1	0	1	0	1	1	0	0
1	1	0	1	1	1	0	0	1	1
1	1	1	0	1	1	0	1	1	1

(b)

#### ERROR IN LISTING 4:

Errors Found in the code full\_adder.sv is missing of & symbol in line no. 10 .

In this code there is an error in line 10 ;

**assign carry = (a & b) | (c(a ^ b));**

This line shows you are trying to multiply c with (a^b) which is incorrect in Verilog . The correct way to represent the carry calculation in a full adder form is by using the AND operation between c and (a^b).

**assign carry = (a & b) | (c & (a ^ b));**

#### ERROR IN LISTING 5:

- In this code there is an error in Line 12:
- In the full adder module, the output port carry1 is written, but it hasn't been declared in the testbench. So , It should be written as follows:

**logic carry1**

- In Lines 18, 20, 22, 24, 26, 28, 30, and 32 there is inconsistency in the variable naming. Some **variables** are assigned using a, b, and c, while others are assigned using a1, b1, and c1. We should use either a, b, and c or a1, b1, and c1 throughout the testbench.
- And also we have added the begin and **end** to show the wave.
- We have added **\$monitor** function which printout the signal values every time they change on the Transcript Window

(c)

Corrected codes are :

**full\_adder.sv**

```
module full_adder(  
    input logic a,  
    input logic b,  
    input logic c,  
    output logic sum,  
    output logic carry  
);  
    assign sum = (a ^ b) ^ c;  
    assign carry = (a & b) | (c & (a ^ b));  
endmodule
```

**full\_adder\_tb.sv**

```
module full_adder_tb();  
    logic a;  
    logic b;  
    logic c;  
    logic sum;  
    logic carry;  
    full_adder UUT(  
        .a(a),  
        .b(b),  
        .c(c),  
        .sum(sum),  
        .carry(carry));  
endmodule
```

initial

begin **// Provide different combinations of the inputs to check validity of code**

a = 0; b = 0; c = 0;

#10;

a = 0; b = 0; c = 1;

#10;

a = 0; b = 1; c = 0;

#10;

a = 0; b = 1; c = 1;

#10;

a = 1; b = 0; c = 0;

#10;

a = 1; b = 0; c = 1;

#10;

a = 1; b = 1; c = 0;

#10;

a = 1; b = 1; c = 1;

#10;

\$stop;

end

initial

begin **/\*the following system task will print out the signal values**

**every time they change on the Transcript Window \*/**

\$monitor("sum1=%b, a=%b, b=%b, c=%b", sum1,a1,b1,c1);

end

endmodule

## **QUESTION # 2**

System Verilog Codes are :

### **full\_adder.sv**

```
module full_adder(  
    input logic a,  
    input logic b,  
    input logic c,  
    output logic sum,  
    output logic carry  
);  
    assign sum = (a ^ b) ^ c;  
    assign carry = (a & b) | (c & (a ^ b));  
endmodule
```

## **QUESTION # 3**

### **full\_adder\_tb.sv**

```
module full_adder_tb();  
    logic a;  
    logic b;  
    logic c;  
    logic sum;  
    logic carry;  
    full_adder UUT(  
        .a(a),  
        .b(b),  
        .c(c),
```

```

.sum(sum),
.carry(carry));
initial
begin // Provide different combinations of the inputs to check validity of code
a = 0; b = 0; c = 0;
#10;
a = 0; b = 0; c = 1;
#10;
a = 0; b = 1; c = 0;
#10;
a = 0; b = 1; c = 1;
#10;
a = 1; b = 0; c = 0;
#10;
a = 1; b = 0; c = 1;
#10;
a = 1; b = 1; c = 0;
#10;
a = 1; b = 1; c = 1;
#10;
$stop;
end
initial
begin /*the following system task will print out the signal values
every time they change on the Transcript Window */
$monitor("sum1=%b, a=%b, b=%b, c=%b", sum1,a1,b1,c1);
end
endmodule

```

# QUESTION # 4

